

## Introduction

16 bit CPU designed using RISC architecture.

The CPU has a 16-bit address bus and a 16-bit data bus.

There are 8 general purpose 16-bit registers, an ALU which can do 9 different operations, an instruction register and an immediate register to hold immediate values.

Each simple instruction is 1-word (16 bits) long with these fields:

- 7-bit opcode (MSBs)
- 3-bit t-register (usually the 2nd operand to the ALU)
- 3-bit s-register (the 1st operand to the ALU)
- 3-bit d-register (LSBs, usually the destination of the ALU operation)

Extended instructions are two words long where the first word has the same format as above and is followed by a 16-bit immediate/literal value.

## The ALU

The ALU takes two 16-bit data inputs and produces a 16-bit data output as well as zero, negative and carry flags. The *aluop* control line specifies which of the 9 available operations to perform.

The 9 available operations are:

1. Addition
2. Subtraction
3. Multiplication
4. Division
5. And
6. Or
7. Xor
8. Nor
9. Nand

## The Register File

The register file contains eight 16-bit general purpose registers.

The *dse1*, *sse1* and *tse1* control lines select which of the eight registers become the d-register, s-register and t-register.

The d-register is generally used as the destination register for ALU operations.

The s- and t-registers are used as ALU sources.

The *regval* input to the ALU is written to a register when one of the *dwrite*, *swrite* or *twrite* lines and enabled.

The source of *regval* is determined by the multiplexer and is controlled by the *regsrc* line.

The options are: from the data bus, from the immediate register, from the ALU output, or from the s-register.

## CODES FOR REGISTERS:

REGISTER	CODE
R0	000
R1	001
R2	010
R3	011
R4	100
R5	101
R6	110
R7	111


## The Immediate Register

It holds the immediate second word from the 2-word instructions.  
It is loaded from the data bus when the *imload* control line is enabled.

## The Instruction Register

The 16-bit IR is loaded from the data bus when the *irload* control line is enabled.  
It just splits out the 16-bits into the 7-bit *opcode* and 3-bit *dsel*, *ssel* & *tssel* control lines.  
It is a single register with a bit-splitter on the right.

### Instruction Register

 


## The Program Counter

The PC is a 16-bit register which is loaded when the *pload* control line is enabled.  
Its new value is controlled by the *pcsel* control line, and allows these inputs:

- PC+1, i.e. increment the PC
- immediate register, used to jump the PC to an absolute address.

PC's new value is chosen by a multiplexer which receives PC+1 using an adder, the immediate register.

## Program Counter

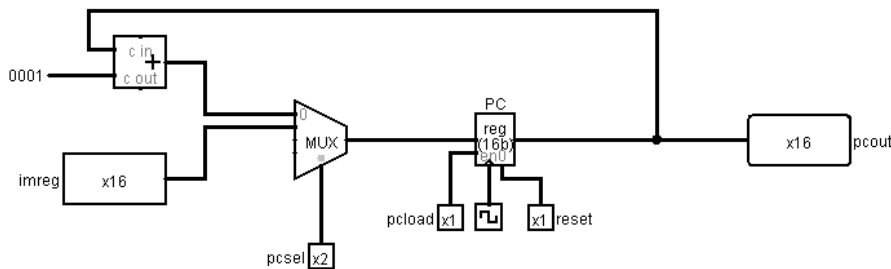

## The Data Bus

Data normally flows from RAM onto the 16-bit data bus and this goes into the immediate register, the IR, and into the multiplexer before the register file.

However, when the *datawrite* control line is enabled, it allows writes out to RAM. There is a controlled buffer which lets the data out onto the bus from the CPU. The multiplexer controlled by the *datasel* line chooses what to write on the data bus i.e the d-register, the t-register or the ALU output.

## The Address Bus

The 16-bit address bus gets its value from one of two inputs controlled by the *addrsel* control line: the PC, the immediate register. This allows such addressing modes as:

- PC: fetch the next instruction
- immediate: fetch from a fixed memory location


## The Microprogram Logic

Each machine-code instruction is interpreted by the microcode logic as several microinstructions. Each microinstruction enables certain control lines which do things as update a register's value, command the ALU to perform a certain operation, fetch a value from memory etc. After each microinstruction, the microcode logic has to determine which next microinstruction to perform.

The microcode unit takes as inputs the current *opcode*. It then outputs all the control lines which control the components and busses: *aluop*, *op2sel*, *datawrite*, *addrsel*, *pcsel*, *pload*, *dwrite*, *irload*, *imload*, *regsrc*, *datasel* and *swrite*.

Internally, the microcode logic is implemented using two ROMs and a micro counter. Each ROM has 256 rows where each row stores a single microinstruction. The control ROM is 32-bits wide, and on each row the bits enable or disable all the CPU control lines for this microinstruction. At present, only 23 out of the 32 bits are used.

## Control Unit

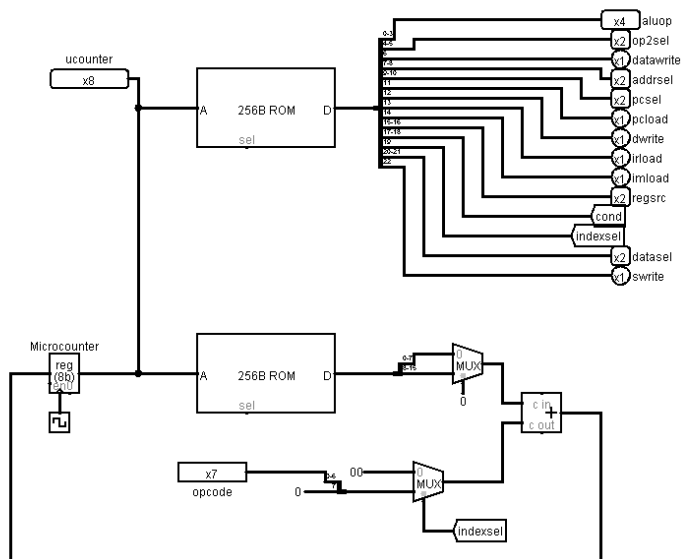

## INSTRUCTION FORMAT:

1 WORD=16 BITS (7+3+3+3=16)

OPCODE (7 bits)	TARGET REGISTER (Rt-3 bits)	SOURCE REGISTER (Rs-3 bits)	DESTINATION REG (Rd-3 bits)
-----------------	-----------------------------	-----------------------------	-----------------------------

## OPCODES:

Instruction	Opcode
Load	0111111
Store	1000001
Add	0000000
Sub	0000001
Mul	0000010
Div	0000011
Rem	0000100
And	0000101
Or	0000110
Xor	0000111
Nand	0001000
Nor	0001001
Move	1000110

## CONTROL SIGNALS FOR INSTRUCTIONS:

### **Fetch:**

addrsel=pc, irload=1, pload=1, ptsel=pc

### **ALU operations on Rd, Rs, Rt:**

aluop=add, op2sel=treg, dwrite=1, regsrc=aluout

Similarly for other ALU operations also.

### **Load Rd, immmed:**

addrsel=pc, dwrite=1, regsrc=databus

### **Store Rd into address from immmed:**

addrsel=pc, imload=1, addrse=immed, datawrite=1, dataset=dreg

### **Move Rd, Rs:**

addrsel=pc, dwrite=1, regsrc=sreg

## SAMPLE PROGRAM:

```
load R0,6           // loads 6 into R0
load R1,2           //loads 2 into R1
sub R0,R0,R1        // R0 <- R0 - R1   R0=6-2=4
mul R0,R0,R1        // R0 <- R0*R1   R0=4*2=8
add R0,R0,R1        // R0 <- R0 + R1   R0=8+2=10
store R0, f         // stores value of R0 in address 000f in the RAM.
```

## HEXADCIMAL CODE:

The following is the hexadecimal code to the above code to be given as input in the RAM in the main of CPU.circ.

<u>RAM ADDRESS</u>	<u>HEX CODE</u>		
0000:	7e00	load R0,6	// loads 6 into R0
0001:	0006	Value to be loaded	//6
0002:	7e01	load R1,2	// loads 2 into R1
0003:	0002	Value to be loaded	//2
0004:	0240	sub R0,R0,R1	// R0 <- R0 - R1   R0=6-2=4
0005:	0440	mul R0,R0,R1	// R0 <- R0*R1   R0=4*2=8
0006:	0040	add R0,R0,R1	// R0 <- R0 + R1   R0=8+2=10
0007:	8200	store R0, a	// stores value of R0 in address 000f in the RAM.
0008:	000f		//Address where the value of register has to be stored